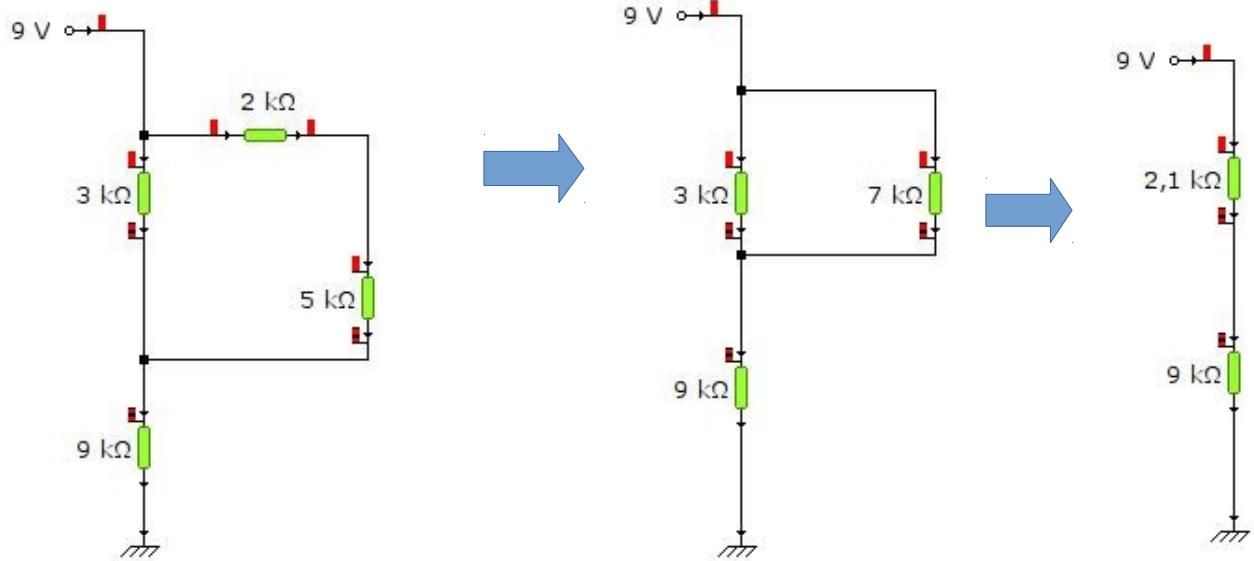


## Combinational circuits.


How to calculate the equivalent resistance?. And then, current and power.

### Example 1




$$I = \frac{V}{R} = \frac{9V}{11,1\text{ k}\Omega} = 0,81\text{ mA} \quad P = VI = 9V \cdot 0,81\text{ mA} = 7,29\text{ mW}$$

### Example 2

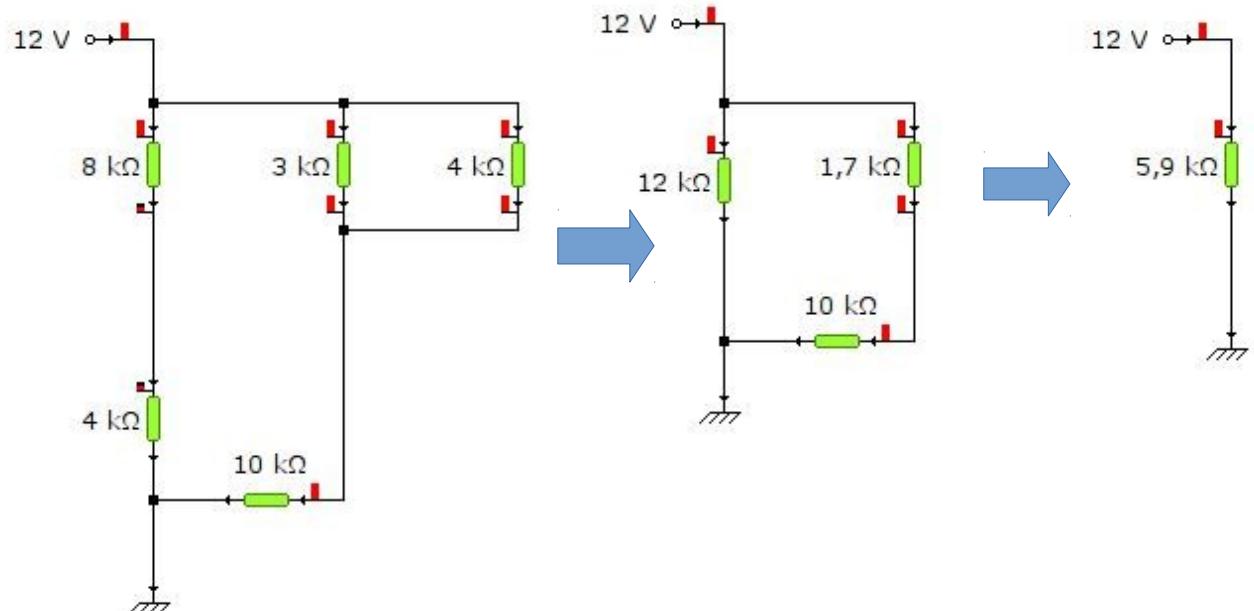

$$I = \frac{V}{R} = \frac{12V}{5,9\text{ k}\Omega} = 2,03\text{ mA} \quad P = VI = 12V \cdot 2,03\text{ mA} = 24,36\text{ mW}$$

### Example 3

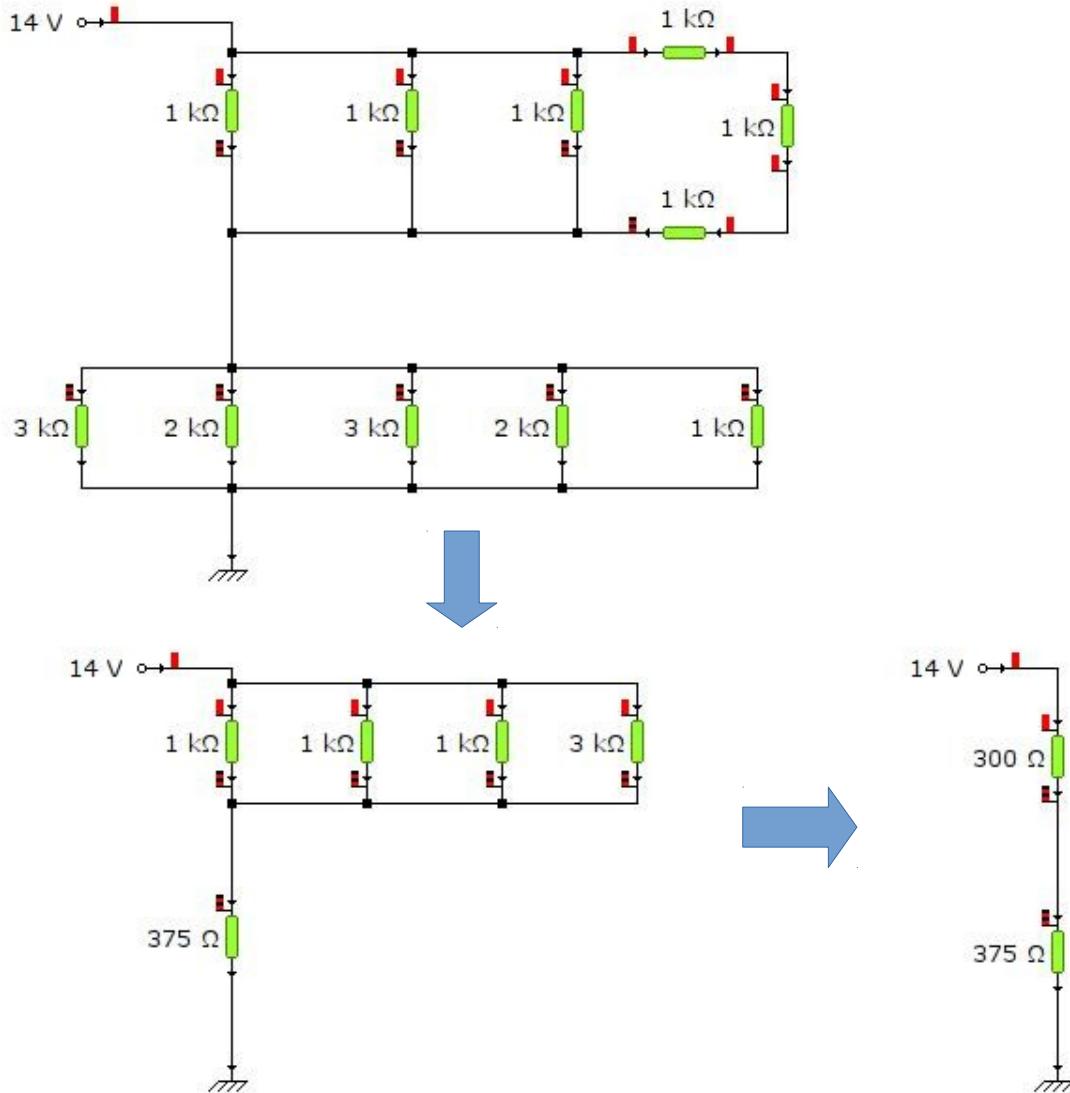

$$I = \frac{V}{R} = \frac{14V}{675\Omega} = 20,74\text{ mA} \quad P = VI = 14V \cdot 20,74\text{mA} = 290,37\text{mW}$$

### Example 4

